

Single phase Unity Power Factor Rectifier using Scalar Control Technique



A G Vishal Anand

Neeraj Gupta

V Ramanarayanan

Department Of Electrical Engineering
Indian Institute of Science
Bangalore
India




Agenda


- Introduction
- Resistance emulation
- Hardware Implementation
- Steady State stability criterion
- Small signal analysis
- Simulation & experimental results




Diode Bridge Rectifier

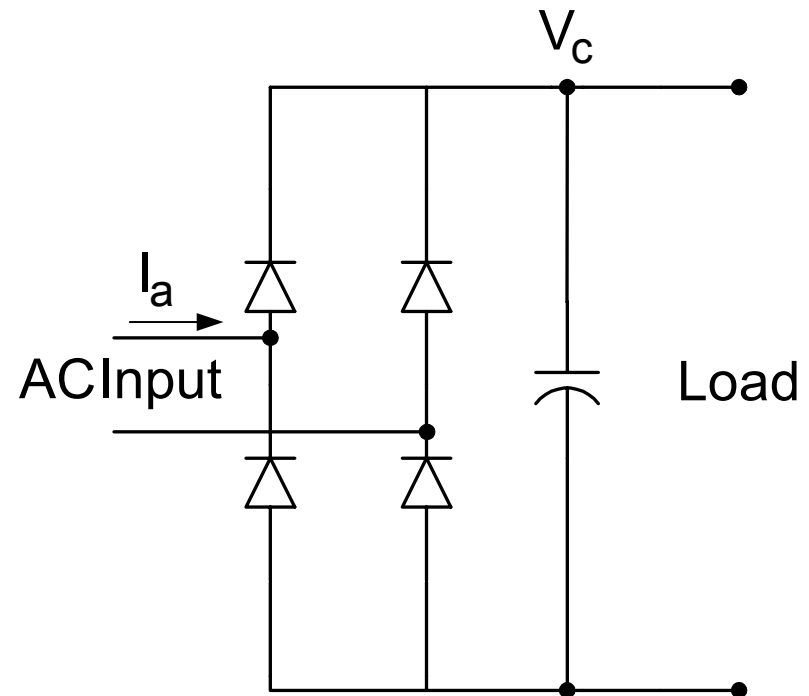- Peak current drawn from the AC source with high harmonic content.
- Higher current stresses on the devices on account of the above problem.



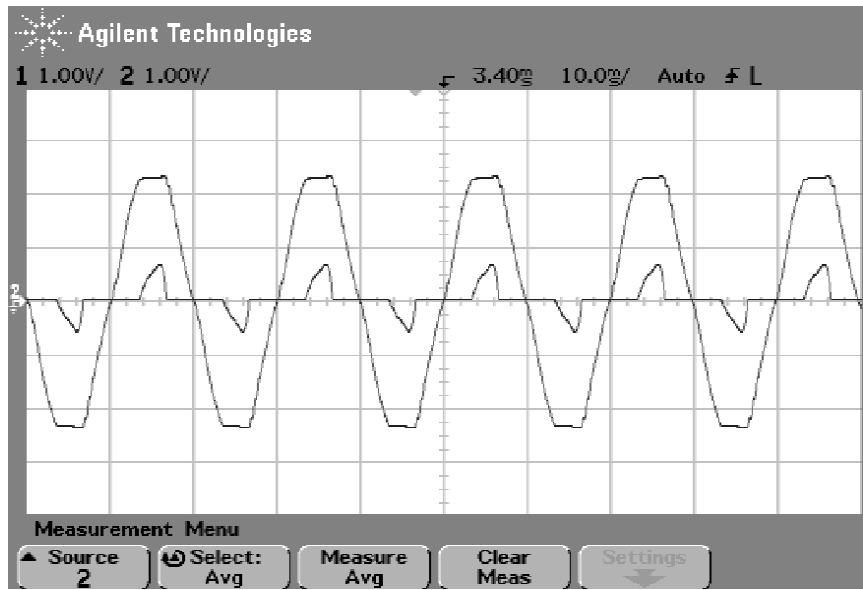

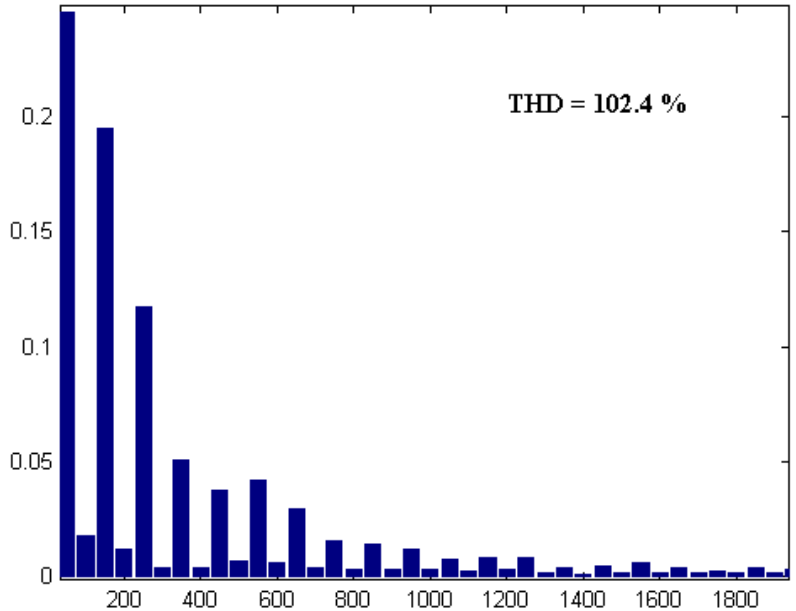Capacitive filter – Input Voltage & Input Current





Capacitive filter - FFT of Input Current




Passive Solution – LC filter

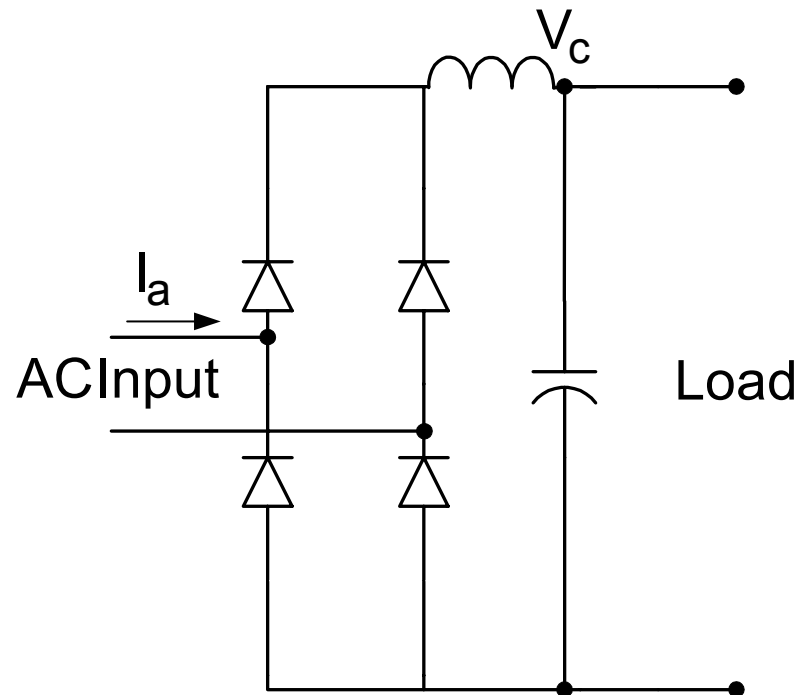- Harmonic content still observed in the input current.
- DC voltage not regulated which's needed in some applications.
- Need for active solution.



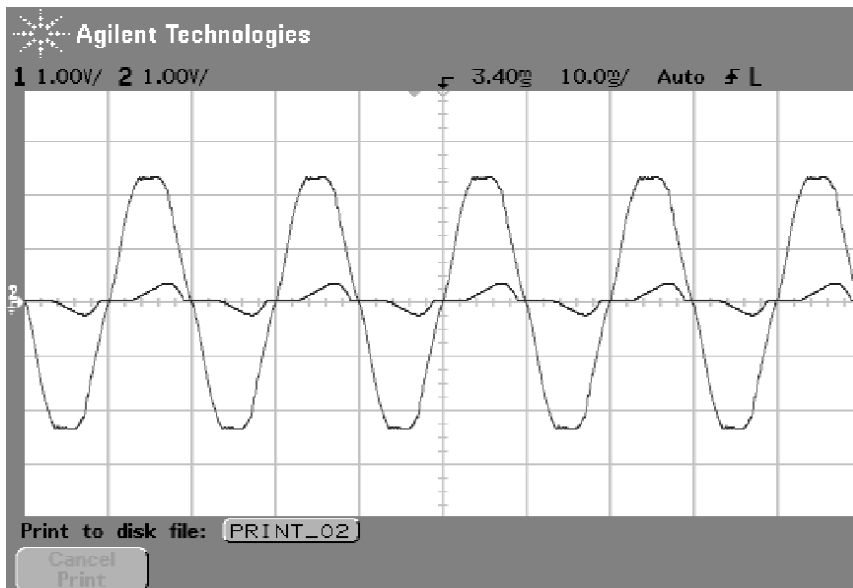

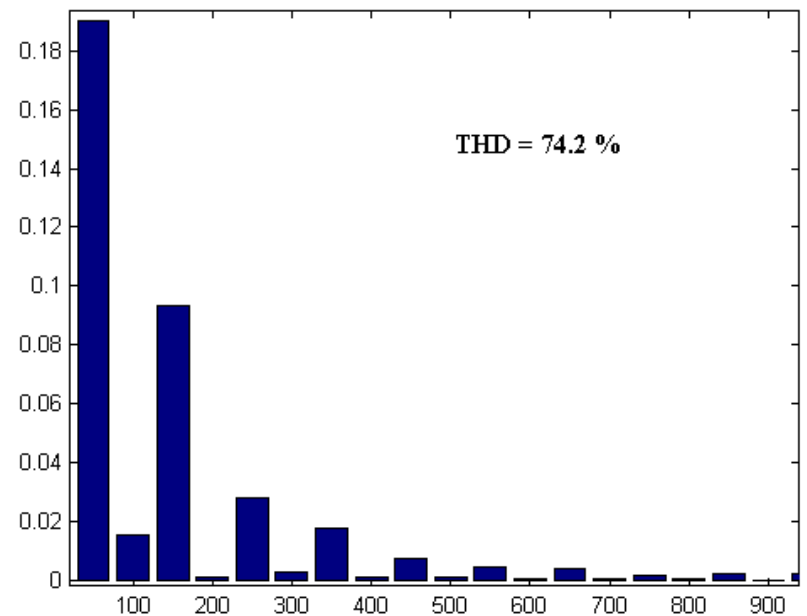Passive filter solution – Input Voltage & Input Current



Passive filter solution – FFT of Input Current




Active Solution – Control Objectives

- Sinusoidal input current in phase with input voltage.
- Regulated DC bus voltage.
- Controlled variables – I_{in} , V_{dc}




Resistance Emulation

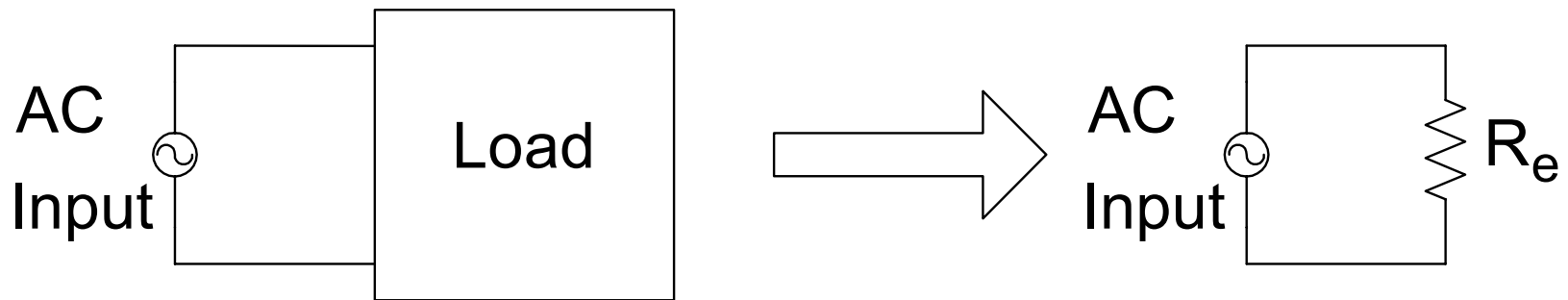

- R_e controls the amount of real power drawn from the source.
- Extension of the same concept gives rise to Impedance Emulation.



Generalized Resistance Emulator

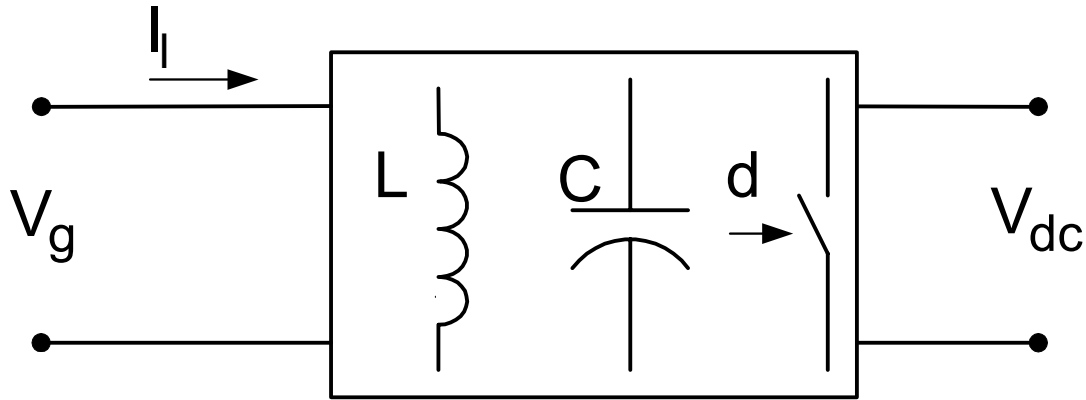

$$V_g = f(d)V_{dc}$$

$$V_g = I_l R_e$$





Generalized Control Law

$$f(d)V_{dc} = I_l R_e$$


$$\Rightarrow f(d) = g(I_l)$$

Many Strategies exist based on the above control law


- Average current mode control
- Peak current mode control
- Non-linear carrier control



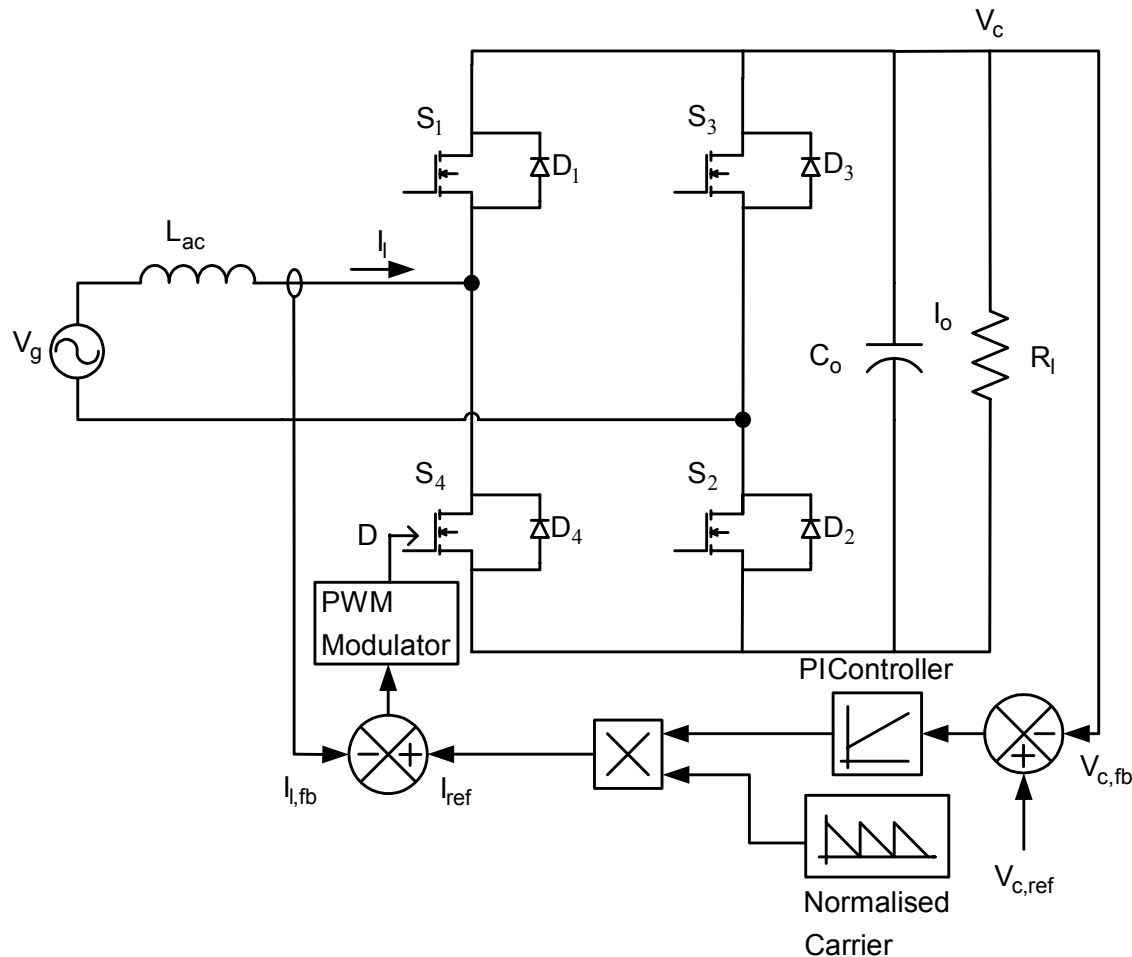Hardware Implementation of Scalar Control



Instantaneous model of the converter

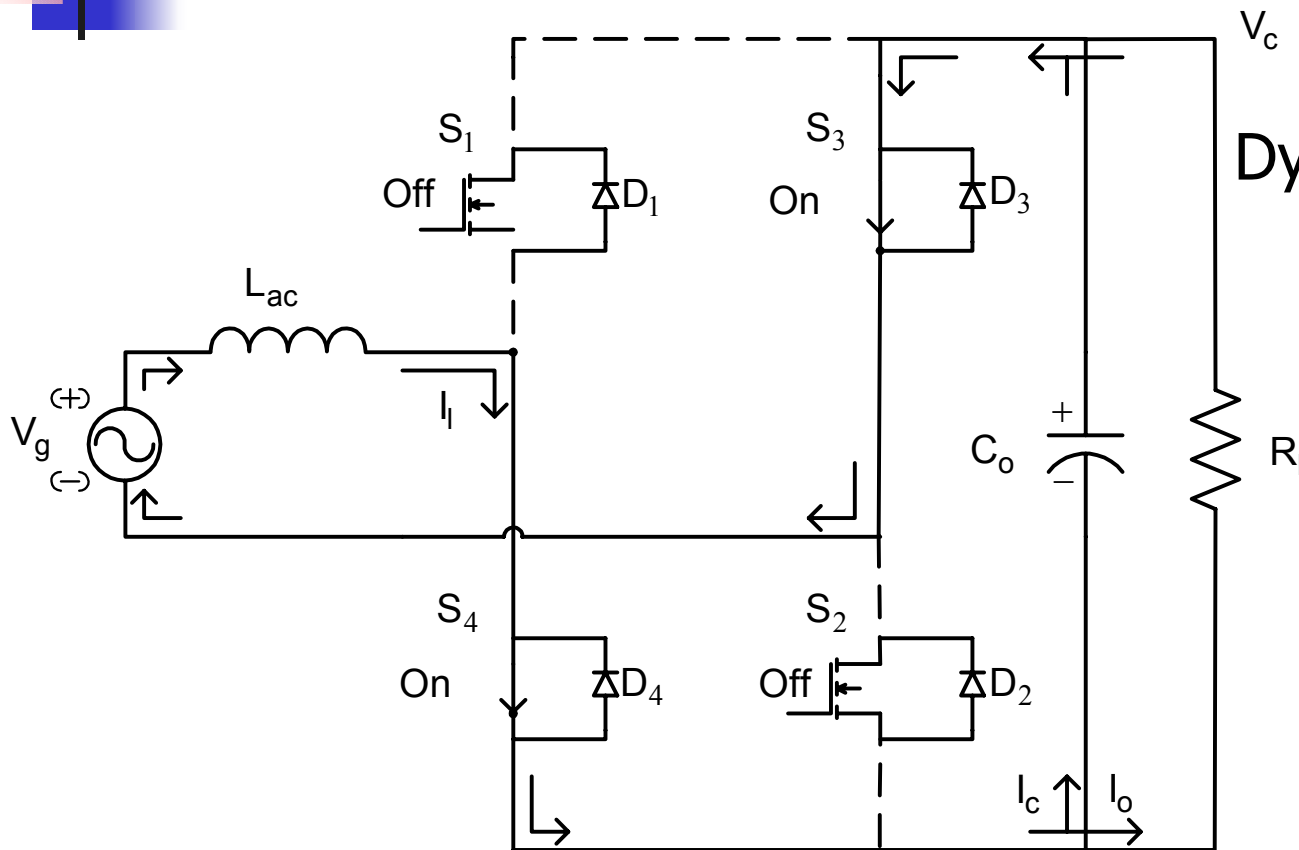

Dynamic Equations


$$v_l = V_g + v_c$$

$$i_c = -i_l - i_o$$

'ON' State Equivalent Circuit



Contd.

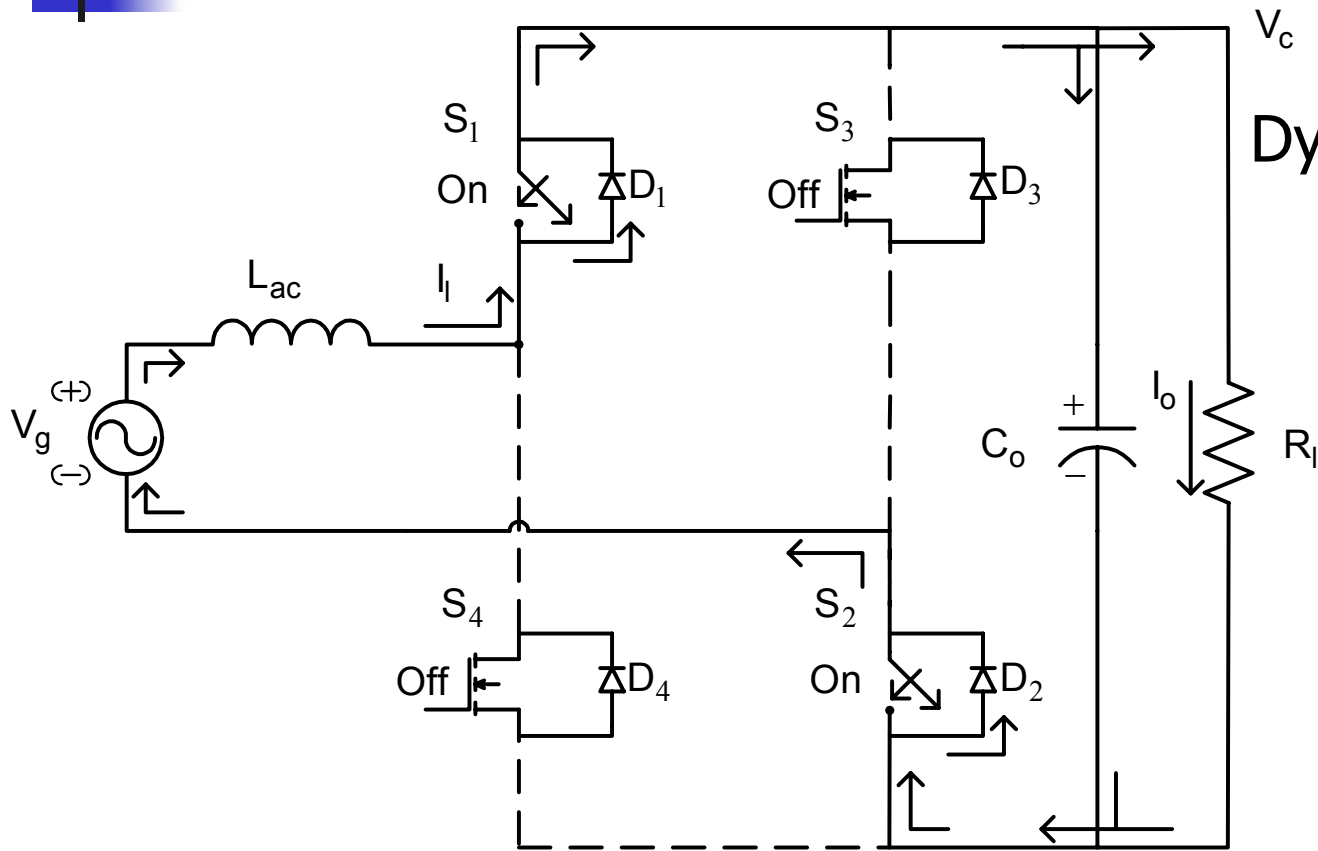

Dynamic Equations

$$v_l = V_g - v_c$$

$$i_c = i_l - i_o$$

'OFF' State Equivalent circuit



Application of Resistance Emulation to Scalar Control

- Converter Characteristic :

$$d = \frac{1}{2} \left[1 - \frac{V_g}{V_{dc}} \right]$$

- Resistance Emulation Characteristic :

$$V_g = I_l R_e$$

- Control Law :

$$d = \frac{1}{2} \left[1 - \frac{I_l R_e}{V_{dc}} \right]$$



Duty ratio command generation

$$d = \frac{1}{2} \left[1 - \frac{I_l R_e}{V_{dc}} \right]$$

Current reference, $I_{ref} = \frac{V_{dc}}{R_e} = \frac{V_m}{R_s}$


$$\therefore d = \frac{1}{2} \left[1 - \frac{I_l R_s}{V_m} \right]$$

where,

V_m is the output of the voltage controller




Contd.

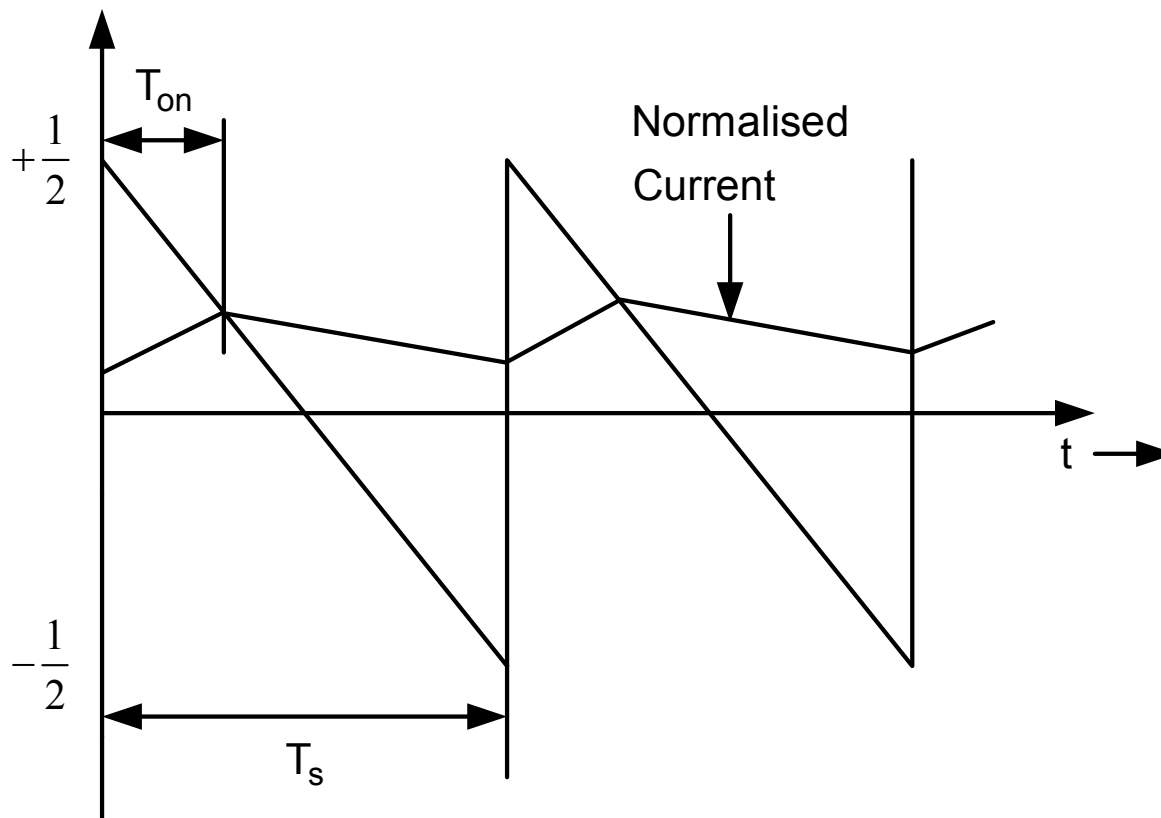

Duty cycle generation based on normalized carrier




Sub-harmonic instability

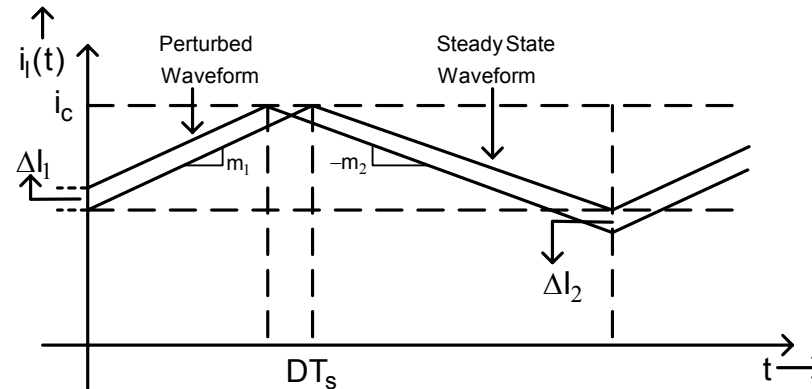

- Linear Peak Current mode control :
Sub-harmonic oscillations set in whenever $D > 0.5$
Problem is solved by addition of compensating ramp.



Contd.

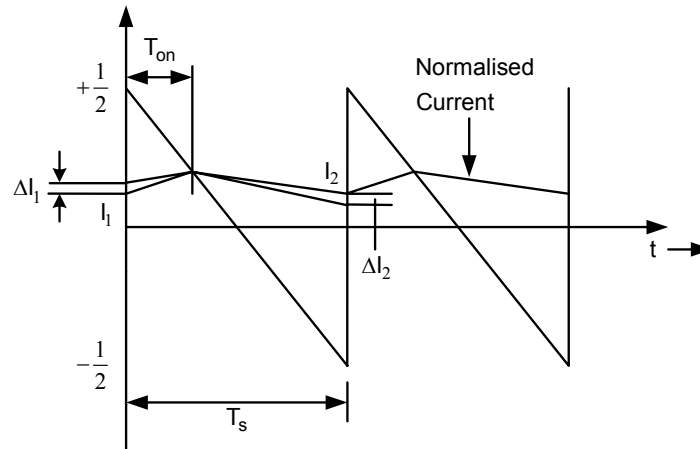


- Perturbation introduced ΔI_1 results in ΔI_2 at the end of the cycle

Stability criterion is $\left| \frac{\Delta I_2}{\Delta I_1} \right| \leq \frac{V_c R_s T_s}{L V_m}$



Small signal model

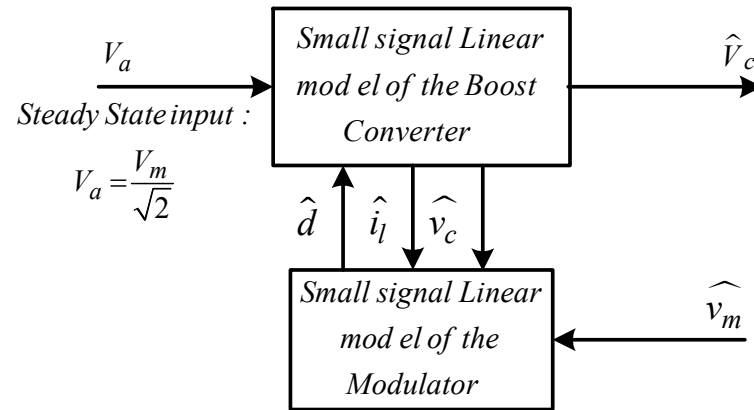

- The small signal model of the converter is obtained by perturbation analysis
- Operating point is fixed based on power balance



Contd.

Perturbation & Linearisation of the averaged model


$$\begin{bmatrix} \frac{d\hat{i}_1}{dt} \\ \frac{d\hat{v}_c}{dt} \end{bmatrix} = \begin{bmatrix} 0 & \frac{2D-1}{L} \\ \frac{1-2D}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} \hat{i}_1 \\ \hat{v}_c \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \hat{v}_g + \frac{1}{2V_m} \begin{bmatrix} \frac{2V_c}{L} \\ -\frac{2I_1}{C} \end{bmatrix} \left[\hat{v}_m (1-2D) + \hat{i}_1 R_s \right]$$

On solving the above equations we get,

$$\begin{bmatrix} \frac{d\hat{i}_1}{dt} \\ \frac{d\hat{v}_c}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{V_c R_s}{V_m L} & \frac{2D-1}{L} \\ 0 & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} \hat{i}_1 \\ \hat{v}_c \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \hat{v}_g + \begin{bmatrix} \frac{V_g}{V_m L} \\ -\frac{I_c}{CV_m} \end{bmatrix} \hat{v}_m$$



Control Transfer function


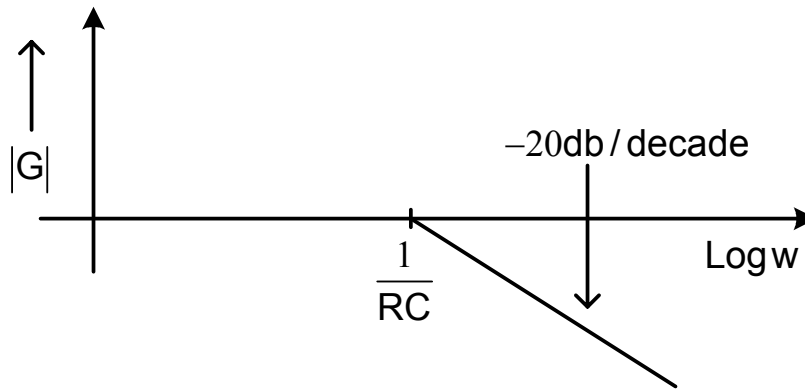


- Output voltage to control variable transfer function

$$\frac{\widehat{v}_c}{\widehat{v}_m} = \frac{V_c}{V_m} \frac{1}{(1 + sRC)}$$



Controller

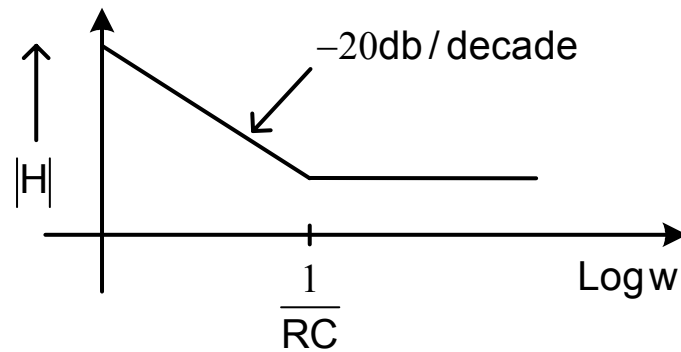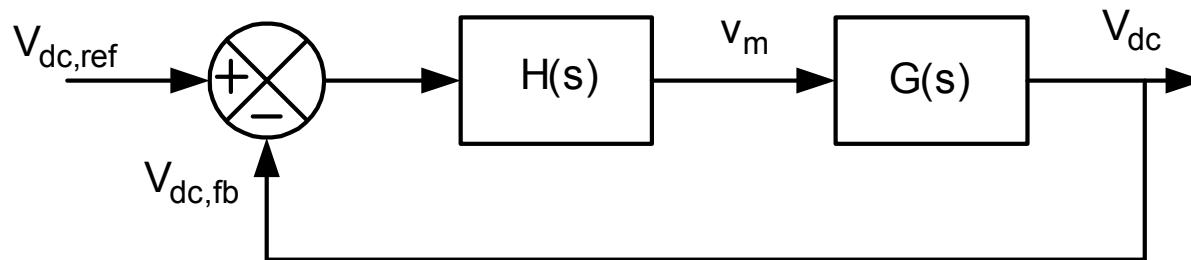

- PI Controller should be sufficient to serve the purpose of zero steady-state error & desired bandwidth





Features of Scalar Control

- Input Voltage need not be measured.
- Control is based on carrier (constant switching frequency) and is simple to realize which is evident from the control transfer function.
- Protection & Parallel operation are added advantages.
- At the cost of one extra active device, the number of passive devices is reduced.





Contd.

- Steady State Stability problem is observed in scalar control.
- The operation is always in CCM.
- Efficiency is slightly higher in this converter on account of the fact that only 2 devices are in the series path of processed power.





Simulation

- System Parameters

Input Voltage range - 100-230V

Output Voltage - 400 V

Rated Power - 750 W


Switching frequency - 19.5 KHz

Line Inductance - 11 mH


Line frequency - 50 Hz




Waveforms

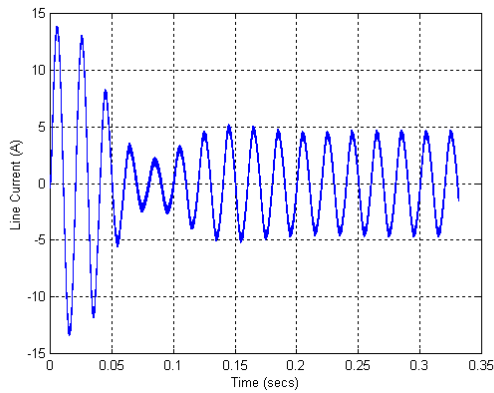

Input current

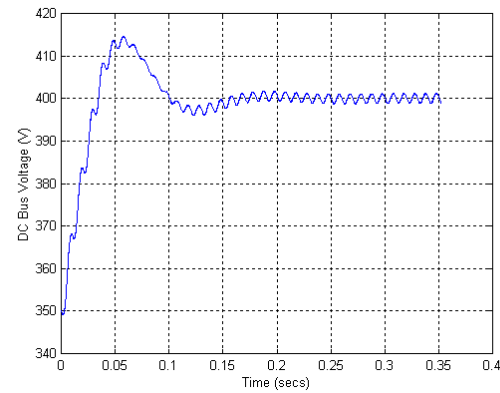


DC Bus Voltage

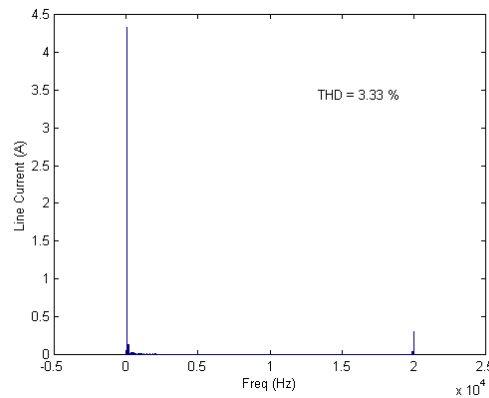


FFT of Input current




Experimental results

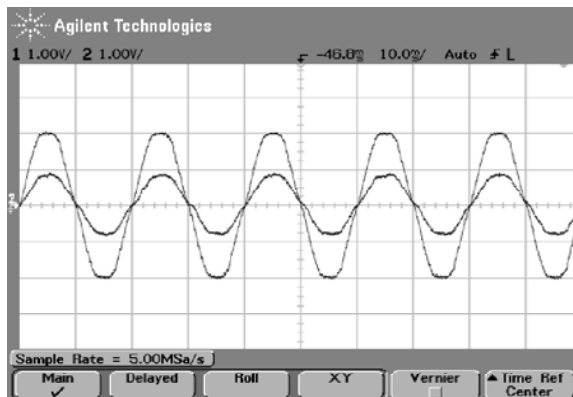

Input Voltage & current

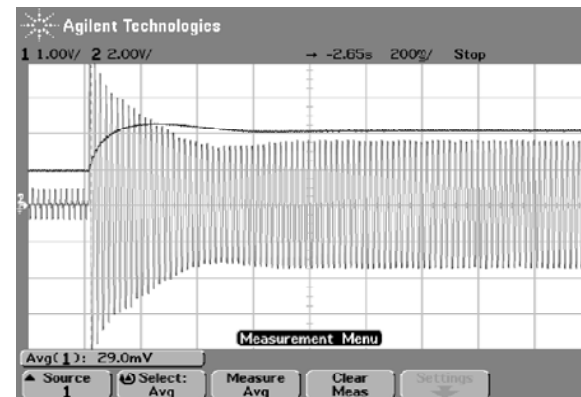


Line current & DC bus voltage

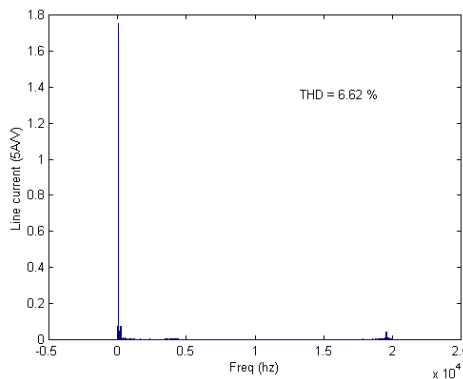


FFT of Input current



Step Response

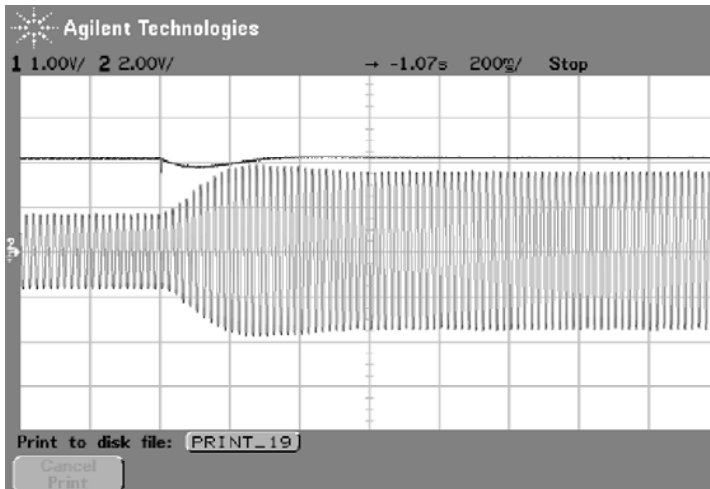

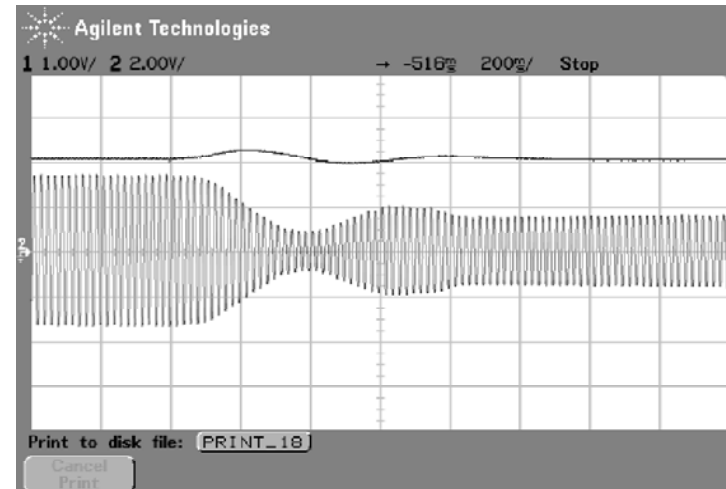
Step change of load from $R=1K$
to $R=300$ ohms




Step change of load from $R=300$ ohms
to $R=1K$



Contd.


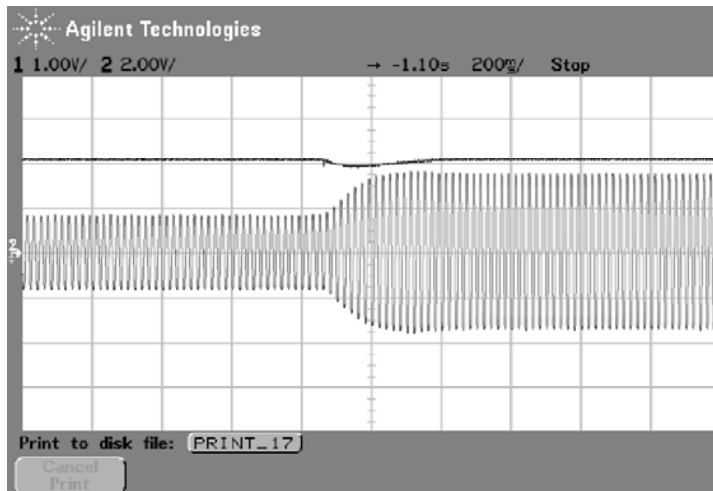


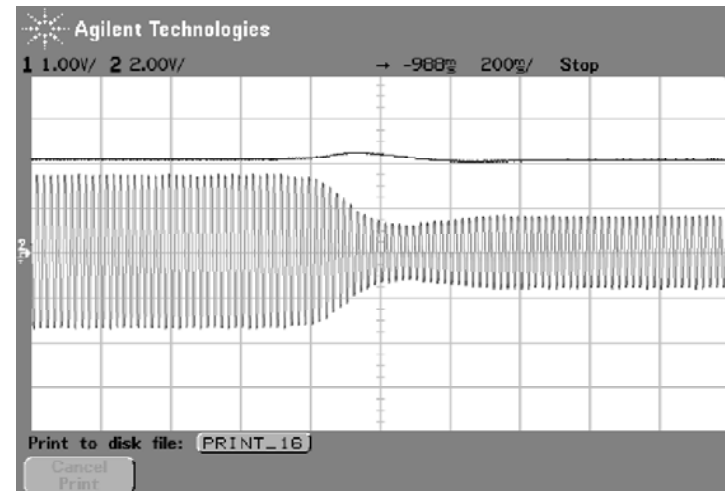
Step change of load from $R=1K$
to $R=300$ ohms



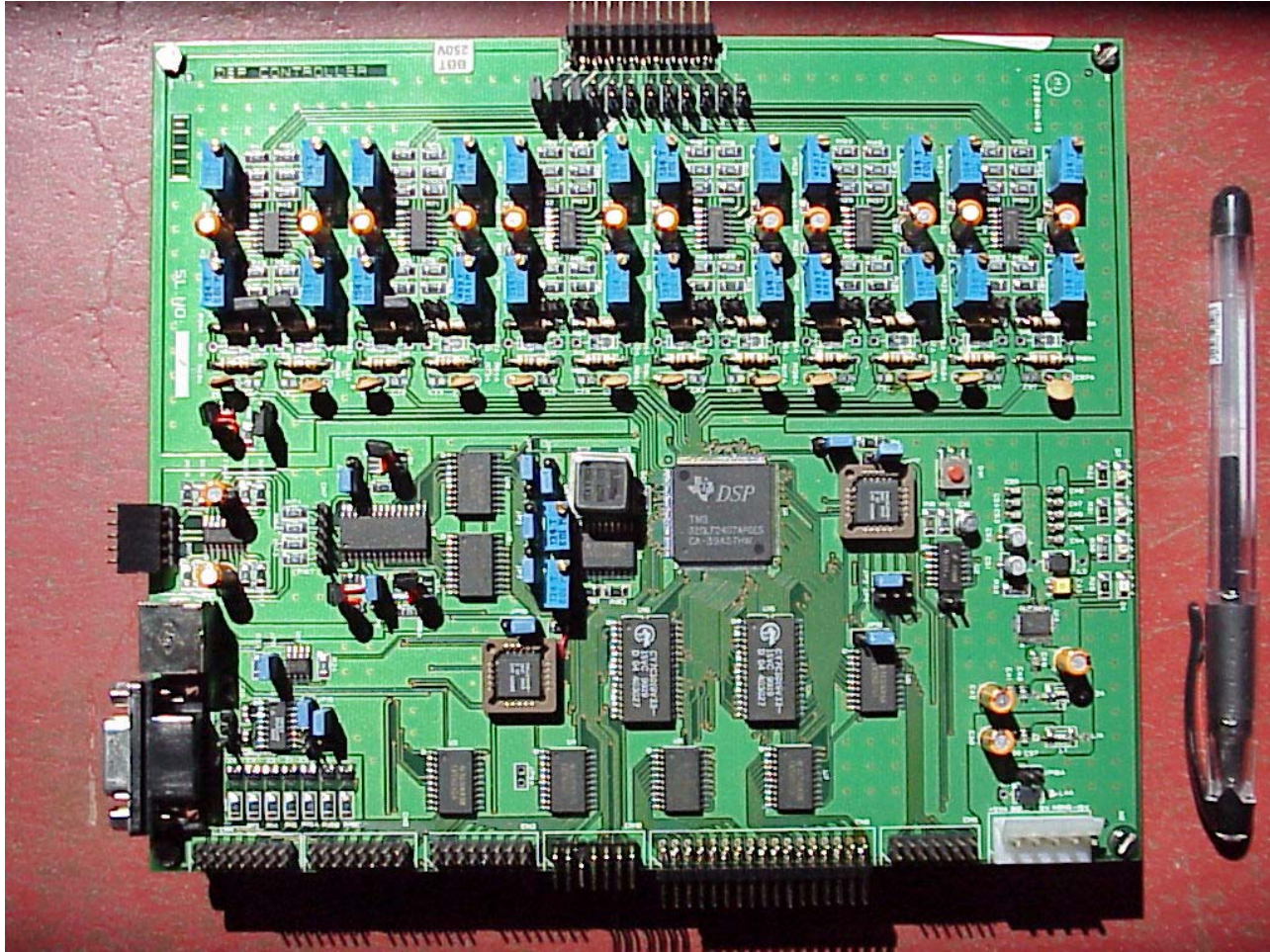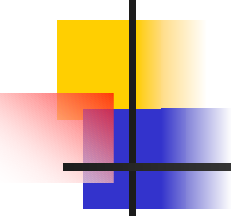Step change of load from $R=300$ ohms
to $R=1K$





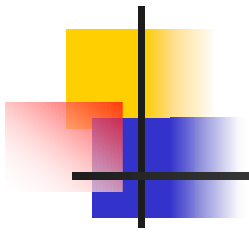

Thank You

